



CE 222 – Computer Organization and Assembly Language (COAL)

Lecture 29

Dr. Asad Mahmood

April 13, 2026

Lecture Outline


- Announcements (Mid re-checking, Assignment and Quiz 4)
- Outline of Previous Lecture:
 - **Chapter 4 – The Processor**
 - 4.5 Multicycle Implementation
- Outline of Today's Lecture:
 - **Chapter 4 – The Processor**
 - 4.5 Multicycle Implementation

Chapter 4

The Processor

Chapter Theme

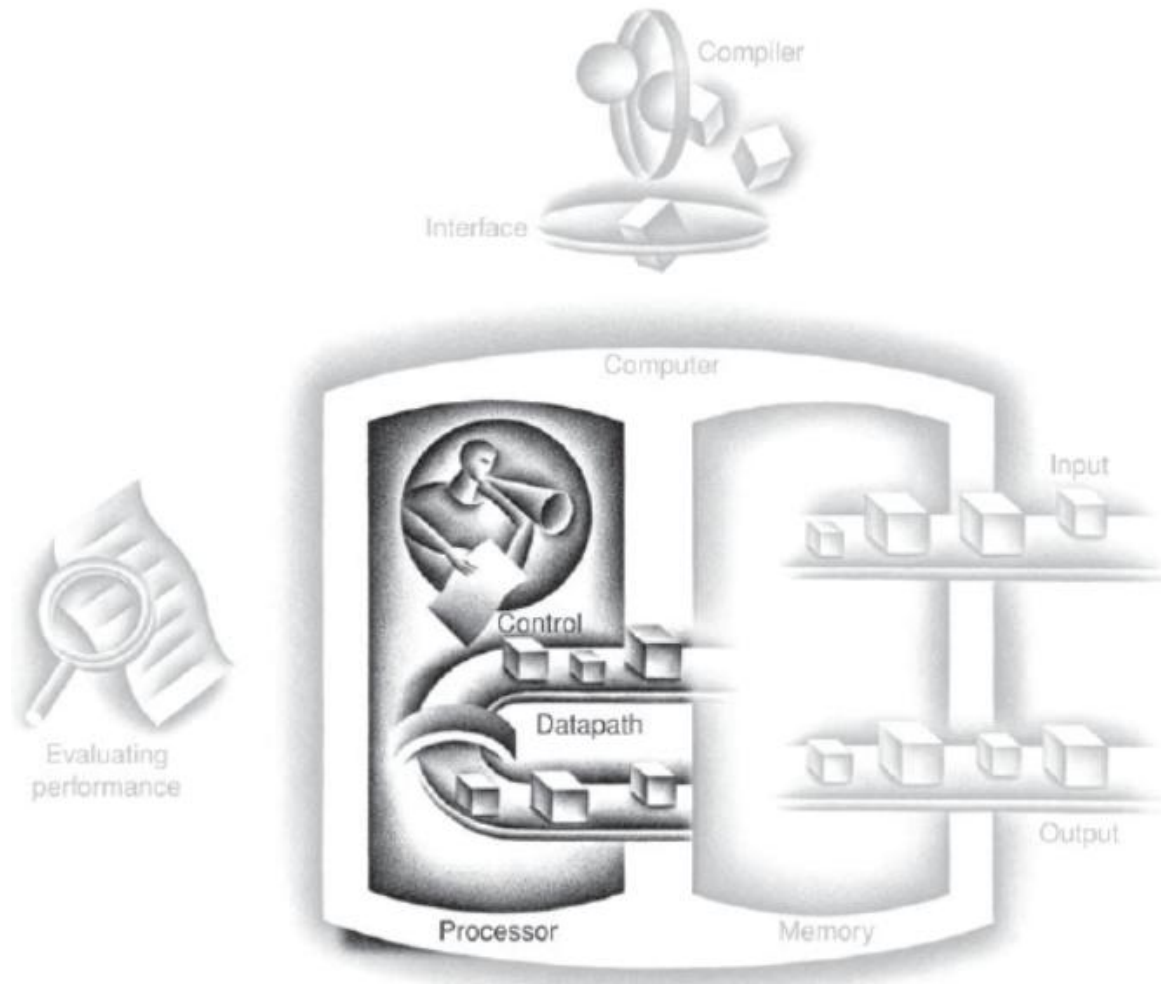The Five Classic Components of a Computer



Chapter Outline

Chapter 4 – The Processor


- 4.1 Introduction
- 4.2 Logic Design Conventions
- 4.3 Building a Datapath
- 4.4 A Simple Implementation Scheme
- 4.5 Multicycle Implementation
- 4.6 An Overview of Pipelining
- 4.7 Pipelined Datapath and Control
- 4.8 Data Hazards: Forwarding versus Stalling
- 4.9 Control Hazards
- 4.10 onwards (self-reading)

Introduction

- Single cycle implementation
- In a multicycle implementation, each *step* in the execution will take 1 clock cycle.
- Multicycle implementation has the following two advantages:
 - Different instructions to execute in different no. of clock cycles
 - Ability to share/re-use functional units within the execution of a single instruction


Multicycle datapath

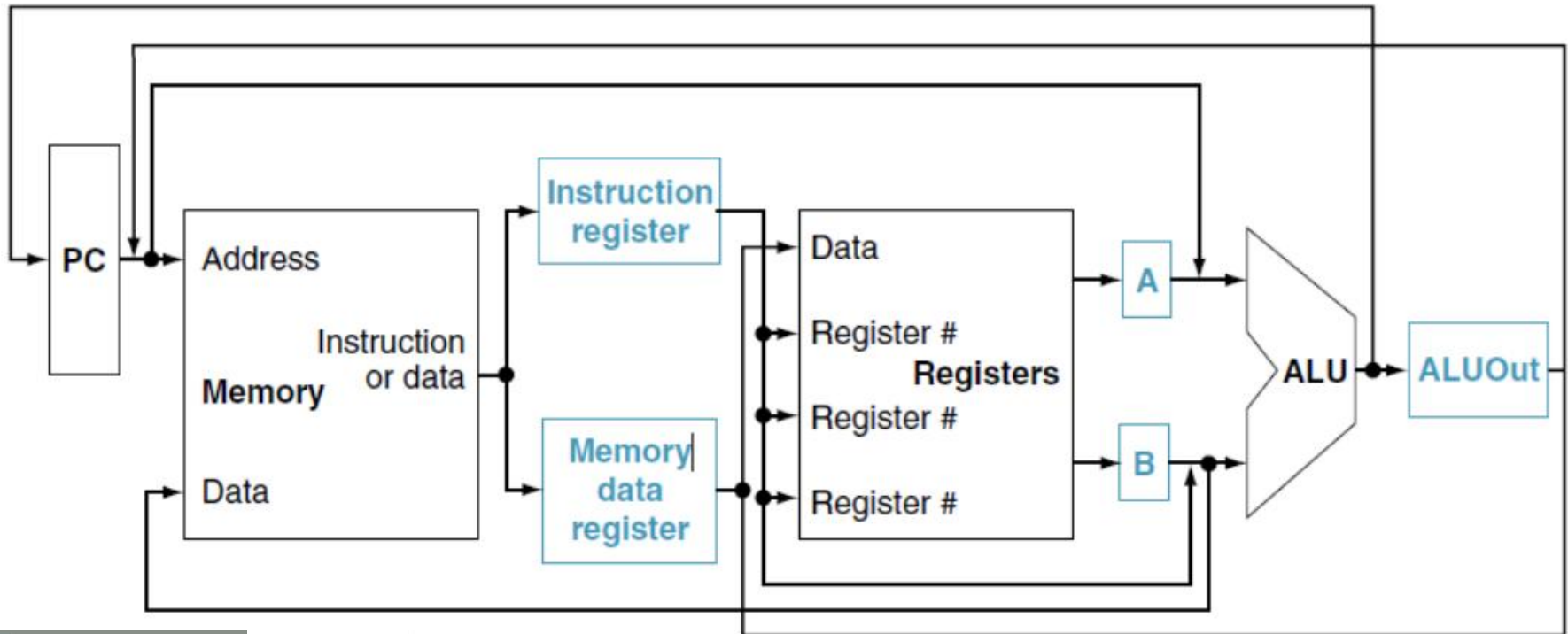- High-level view of the multicycle datapath
- Identify the differences with respect to the single-cycle datapath
- Steps executed in a single clock-cycle in this datapath
- Address of the single memory




Multicycle datapath

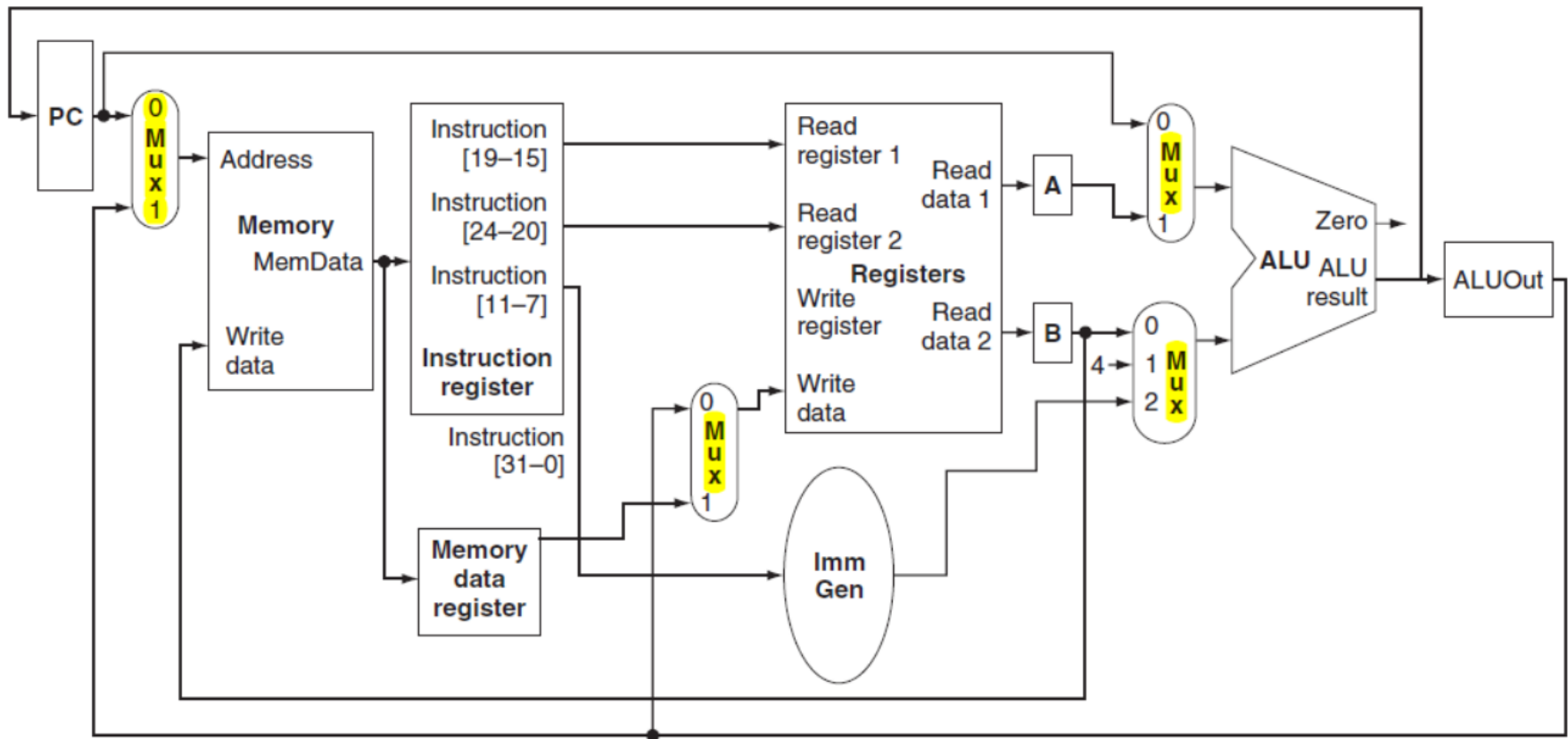- Multicycle datapath with multiplexers
- Size with respect to single-cycle implementation




Multicycle datapath

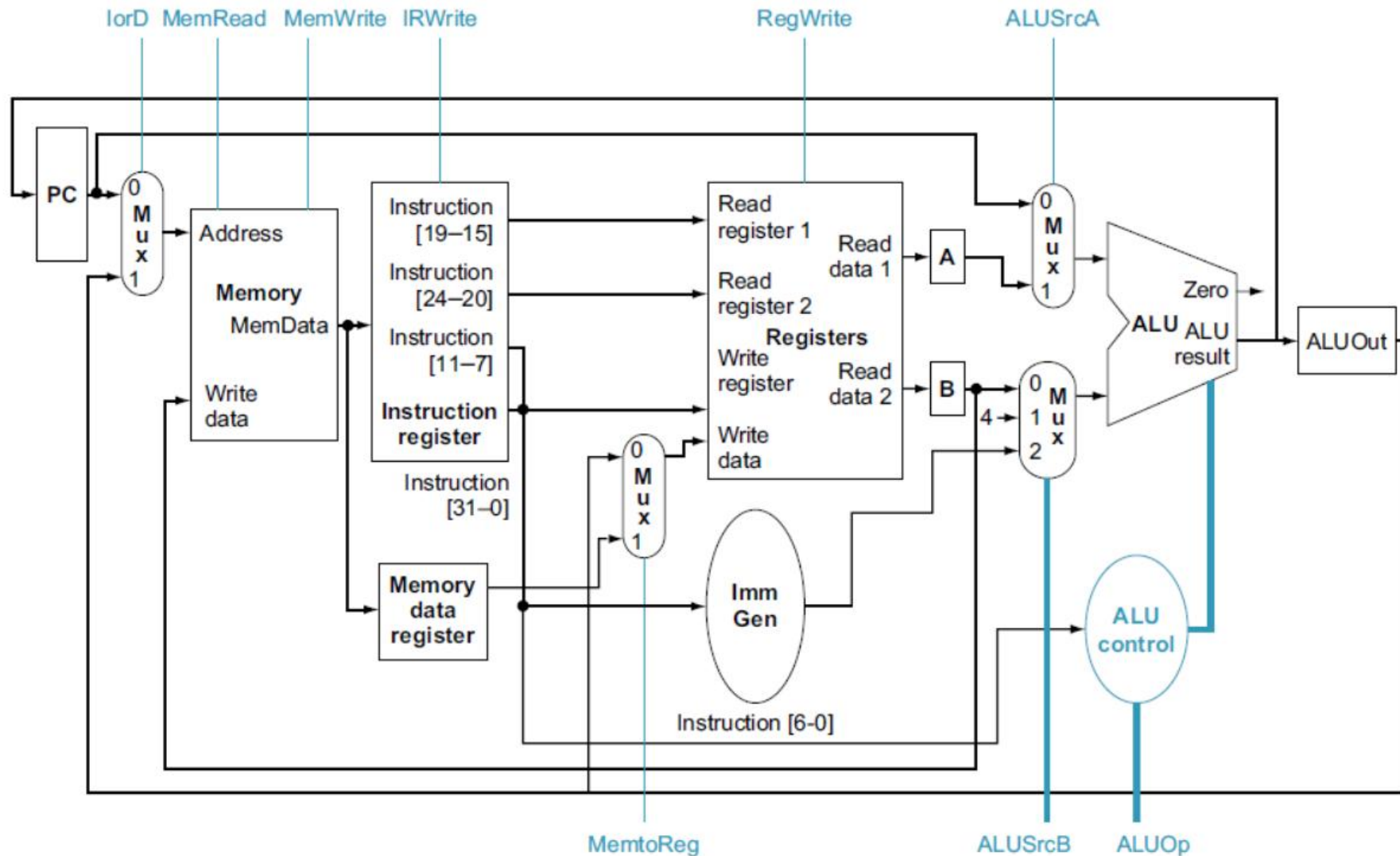- Multicycle datapath with control signals



Multicycle datapath

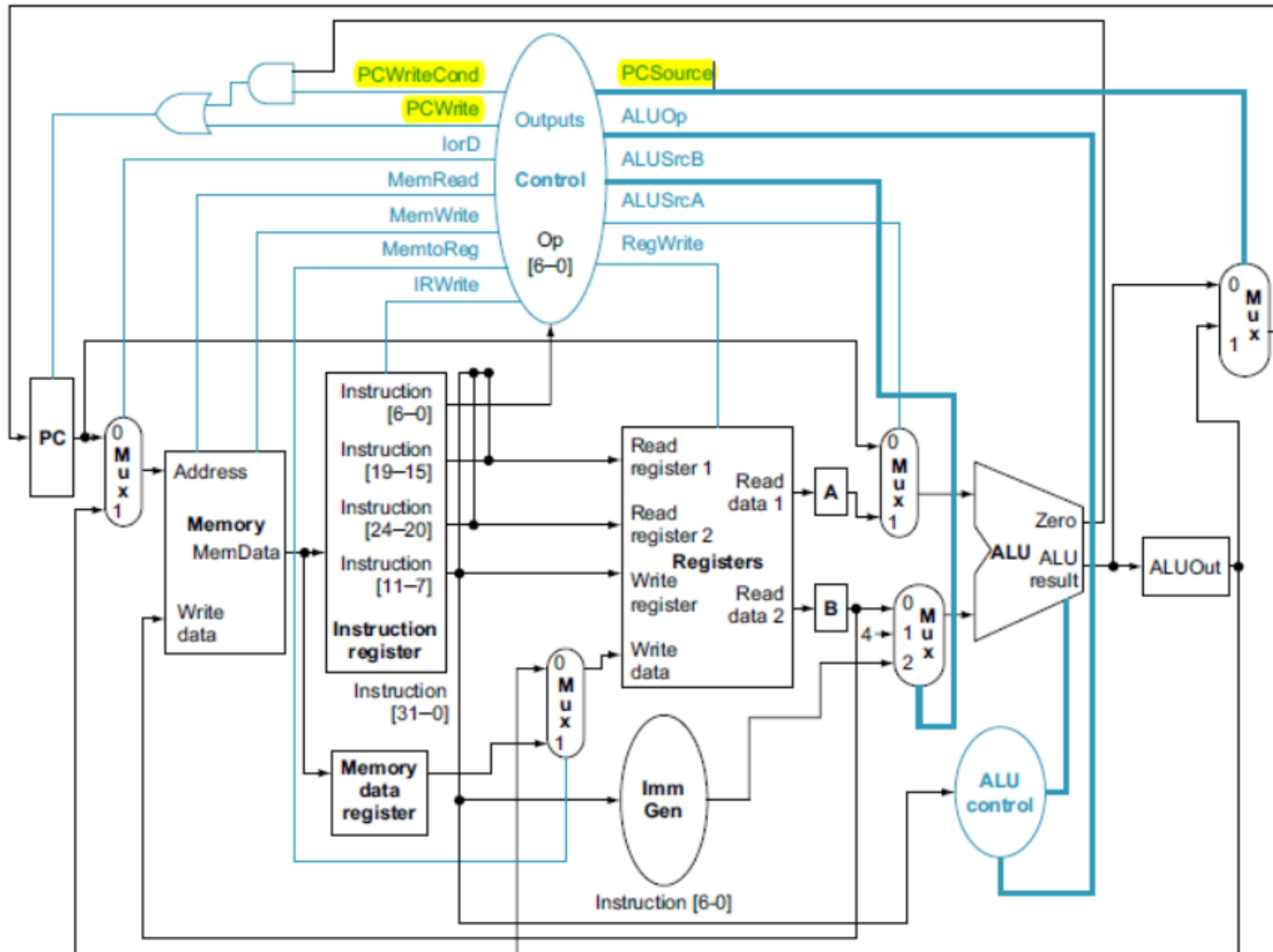- Complete multicycle datapath including support for branch instructions



Multicycle datapath

Actions of the 1-bit control signals

Signal name	Effect when deasserted	Effect when asserted
RegWrite	None.	The general-purpose register selected by the Write register number is written with the value of the Write data input.
ALUSrcA	The first ALU operand is the PC.	The first ALU operand comes from the A register.
MemRead	None.	Content of memory at the location specified by the Address input is put on Memory data output.
MemWrite	None.	Memory contents at the location specified by the Address input is replaced by the value on the Write data input.
MemtoReg	The value fed to the register file Write data input comes from ALUOut.	The value fed to the register file Write data input comes from the MDR.
lorD	The PC is used to supply the address to the memory unit.	ALUOut is used to supply the address to the memory unit.
IRWrite	None.	The output of the memory is written into the IR.
PCWrite	None.	The PC is written; the source is controlled by PCSrc.
PCWriteCond	None.	The PC is written if the Zero output from the ALU is also active.

Actions of the 2-bit control signals

Signal name	Value (binary)	Effect
ALUOp	00	The ALU performs an add operation.
	01	The ALU performs a subtract operation.
	10	The funct field of the instruction determines the ALU operation.
ALUSrcB	00	The second input to the ALU comes from the B register.
	01	The second input to the ALU is the constant 4.
	10	The second input to the ALU is the immediate generated from the IR.
PCSrc	00	Output of the ALU ($PC + 4$) is sent to the PC for writing.
	01	The contents of ALUOut (the branch target address) are sent to the PC for writing.
	10	The jump target address ($IR[25:0]$ shifted left 2 bits and concatenated with $PC + 4[31:28]$) is sent to the PC for writing.

Multicycle datapath

Breaking the Instruction Execution into Clock Cycles

- Let us break instruction execution into a series of steps, where each step taken a single clock cycle
- This division is done such that major components (ALU, Memory, Register File) are only used once per step
- This also helps in keeping the clock cycle small

Multicycle datapath

Breaking the Instruction Execution into Clock Cycles

- Each RISC-V instruction needs from three to five of these steps:
 1. Step1: Instruction fetch step
 2. Step2: Instruction decode and register fetch step
 3. Step3: Execution, memory address computation, or branch completion
 4. Step4: Memory access or R-type instruction completion step
 5. Step5: Memory read completion step
- How many steps for R-type, memory-access, branch instructions?

Multicycle datapath

Step 1: Instruction fetch step

- Fetch instruction and load next instruction address in PC
- Generate appropriate control signals

Control Signal (1 bit)	Value
RegWrite	
ALUSrcA	0
MemRead	
MemWrite	
MemtoReg	
lrd	0
IRWrite	
PCWrite	1
PCWriteCond	

Control Signal (2 bit)	Value
ALUOp	00
ALUSrcB	01
PCSource	00

Multicycle datapath

Step 2: Instruction decode and register fetch step

- Act **optimistically** i.e. read registers and calc. branch address
- Generate appropriate control signals

Control Signal (1 bit)	Value
RegWrite	
ALUSrcA	0
MemRead	
MemWrite	
MemtoReg	
lrd	
IRWrite	
PCWrite	
PCWriteCond	

Control Signal (2 bit)	Value
ALUOp	00
ALUSrcB	10
PCSource	00

Multicycle datapath

Step 3: Execution, memory address computation, or branch completion step

- First step/cycle in which the action is instruction type-dependent
- R-type, memory-access and branch instruction action
- Following tables show control signals for the branch instruction

Control Signal (1 bit)	Value
RegWrite	
ALUSrcA	1
MemRead	
MemWrite	
MemtoReg	
lrd	
IRWrite	
PCWrite	
PCWriteCond	1

Control Signal (2 bit)	Value
ALUOp	01
ALUSrcB	00
PCSource	01

Multicycle datapath

Step 4: Memory access or R-type instruction completion step

- R-type, memory-access and branch instruction action
- Following tables show control signals for the Load-word instruction

Control Signal (1 bit)	Value
RegWrite	
ALUSrcA	
MemRead	1
MemWrite	
MemtoReg	
IorD	1
IRWrite	
PCWrite	
PCWriteCond	